

# ECE 382 LAB 6 PRELAB

Name:

Section:

Documentation:

**NEATLY** wire the appropriate signals to control your motors with the MSP430. Label the MSP430 signals that you use (e.g., TA1.1, P1.2) inside of the chip diagram.

